



RFI Solutions from KHz to GHz


5 Quick & Easy RFI Solutions



Bob Brehm, AK6R
Chief Engineer
Palomar-Engineers.com


PAPA System - September 2018
This presentation available on website
Copyright 2013-2018 Palomar Engineers, Inc.

Are you the **SOURCE** of RFI?

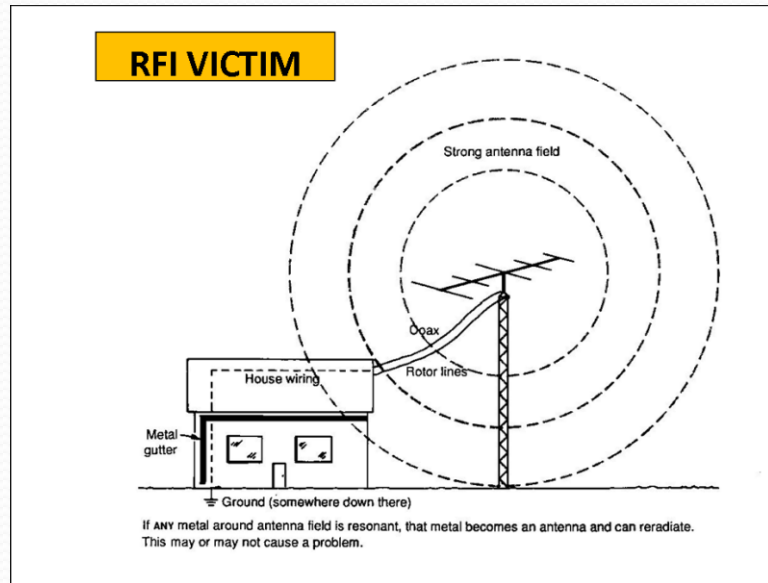

IT'S ALL YOUR FAULT WITH THAT BIG ANTENNA!

Are you a **VICTIM** of local RFI?

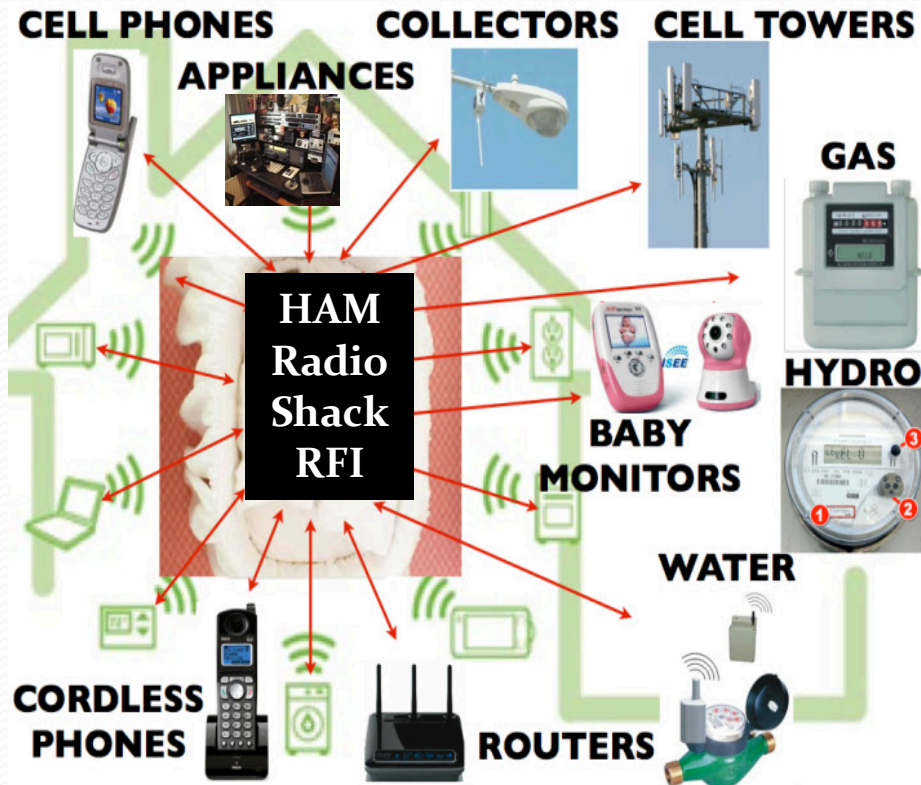

RFI Sources

- Ham Antenna
- Radiating Coax
- Electronic Devices
- Solar Systems
- Grow Lights
- HVAC motor
- Plasma TV
- DSL/Routers
- Switching power Supplies
- Washer/Dryer or other appliances

QRN - High Noise Floor – Weak Signals – NO DX – No fun!

What is RFI?


- *A radio frequency (>100 KHz) disturbance that causes an electrical circuit to function improperly*

Common Sources

- Sunspots, Cosmic noise, Lightning, atmospheric static, AC power lines (**no fix**)
- “Transmitters” -Ham, CB, AM/FM, electronic devices, speed controllers, inverters, switching power supplies, computer electronics, Cable/DSL/Ethernet (**can use filters to fix**)
- Common Victims
 - Any electronic device that malfunctions by acting as an unintended “receiver” of RFI

How do you get RFI?

How RFI is Transferred

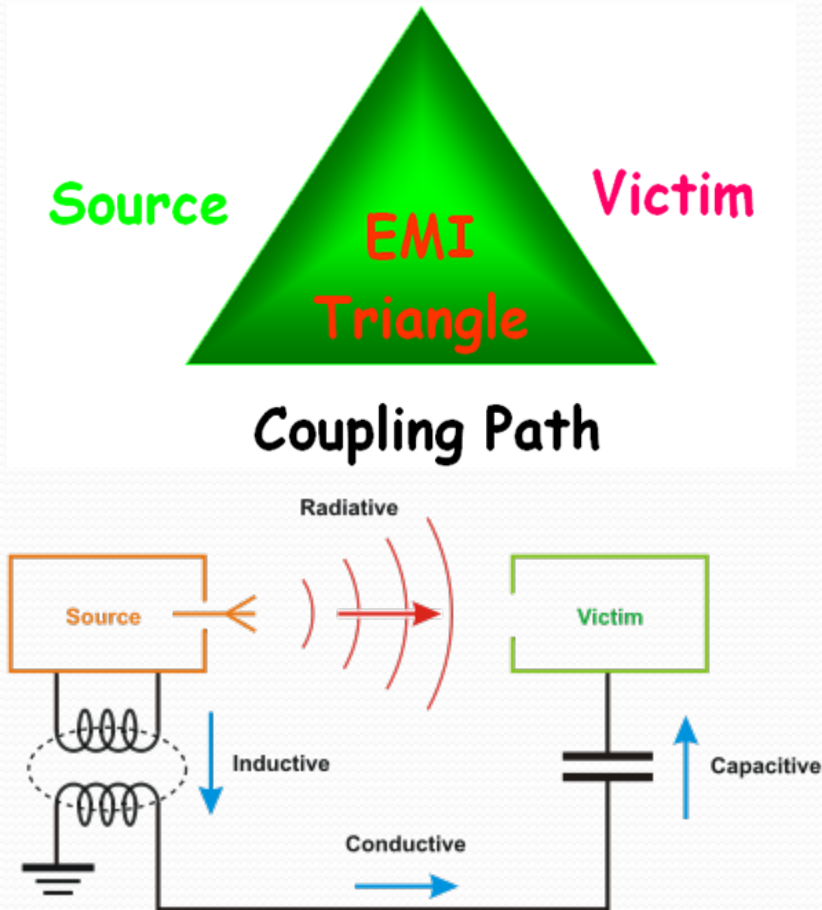

Source (antenna) and **Victim** (antenna) coupled via **Path** (all must be present to have RFI)

Multiple paths are very common:

1. Radiative - air
2. Conductive – wire(s)
3. Inductive - wire
4. Capacitive - wire



How to find the source & path

Typical RFI in your shack/home

- **TX Symptoms** – caused by your transmitter or antenna
 - Hot microphone – RF lip burns, distorted audio
 - Antennas don't tune correctly, high SWR, radiating coax
 - Your voice/transmission causes interference with consumer electronic devices acting as ham radio frequency “receivers” (e.g. computers, TV/audio system, security system, garage door opener, telephone, sprinkler systems, lights, etc.)
 - Wife Alarm goes off
 - **RX Symptoms** – caused by sources outside your radio
 - High receive noise level not due to atmospheric conditions
 - Birdies, chirps, buzzes, clicks, broadband noise on receiver
 - Distorted receiver audio
- “Antennas” & paths

Typical RFI receiving “antennas”

- **AM broadcast, 160-80-60-40-30 meter RFI** – long “antennas” - AC power lines, telephone/DSL lines, satellite/cable coax, long Ethernet cables, antenna feed line coax shield, antenna control/rotor cables, 2nd story ground wires (avoid $\frac{1}{4}$ wavelength ground wires)
- **FM broadcast, 20 meter-UHF transmitter RFI**,– short “antennas” - speaker wires, device interconnect cables, mic cables, short Ethernet cables
- “Antennas” pick up radiated or conducted RFI and a common mode current is induced on ALL unshielded antenna conductors from an RFI SOURCE

So how do we reduce this current?

Curing RFI Issues



I (RFI Current) = E (TX voltage)/ R (Choking resistance)

- Shut down the SOURCE (Set E to zero)
- Choke the PATH (minimize E , increase R)
- Protect the VICTIM (Set R very high)

Objective: Minimize RFI current, I

Trivia Q: Why is current abbreviated with I and not C ?

Using ferrites to cure RFI



Ferrite Fundamentals

How to Select,

Buy,

Configure,

and Apply



Ferrite Topologies (Shapes)



Slip On Bead



Snap On Bead



Toroid or Ring




Fuzzy Ferret – not!

CHARACTERISTICS

- Cheap, easy to install, suppress RFI from 100 KHz - 2 GHz
- Work on all conductive paths (antenna feed line, AC/DC, I/O cables)
- Lots of options in size, shape to suppress most RFI path currents
- Are effective if you understand how ferrites work, how to choose the correct ferrite and where to install the ferrite for a particular RFI problem

Ferrite characteristics can be used to reduce RFI common mode current

Ferrite resistors add in series

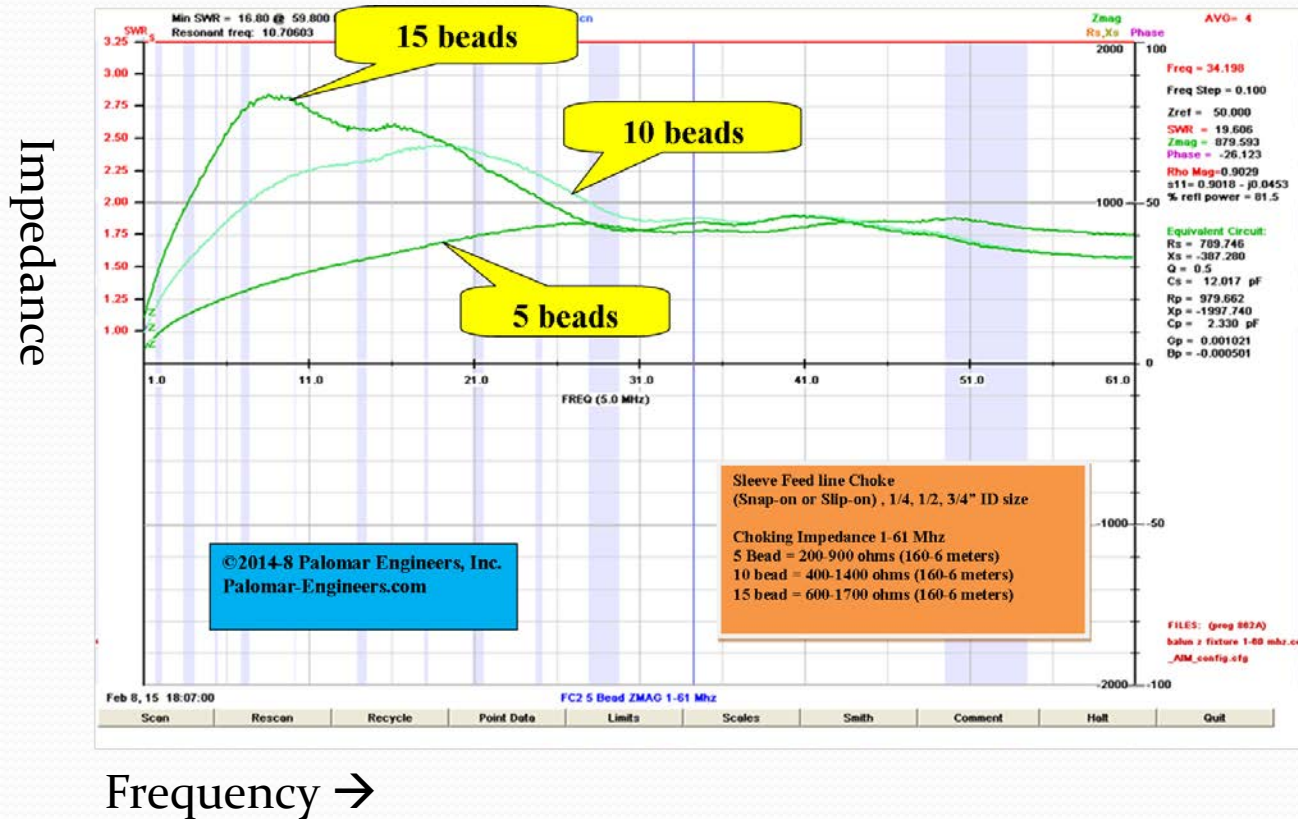

More beads =

higher choking R
(up to 30 MHz)

At 7 MHz:
5 beads = 400Ω

10 bead = 1000Ω

15 beads = 1600Ω



$$\text{Impedance (Z)} = \text{Resistance} \pm \text{Reactance}$$

Ferrite resistors increase as (turns)²


- If 1 turn = R, 2 turns = 4 x R, 3 turns = 9 x R
- More R = less RFI wire current = less RFI radiated from wire or induced into wire. ($I=E/R$)
- **General rule: choking R > 10X line impedance**
- (e.g. > 500 Ω for 50 Ω cable but 5000 Ω is 10x better)



7 MHz: 100 Ω




900 Ω

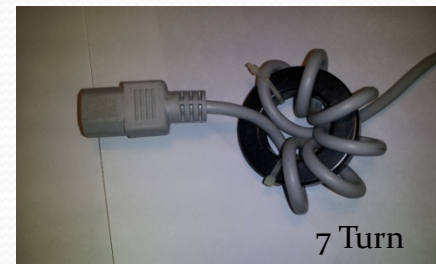

2500 Ω

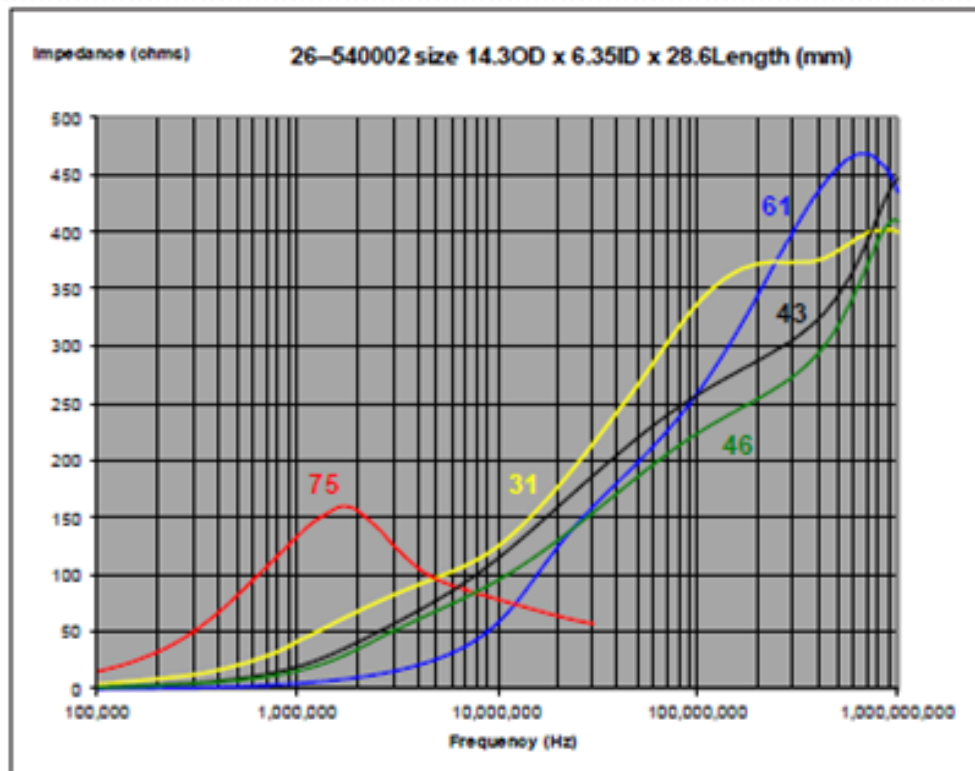Question: How do we choose the correct ferrite for the RFI frequency?

Ferrite Mix determines frequency range of effectiveness



Mix = chemical formula of the iron oxide with manganese-zinc (31, 75) or nickel-zinc (43, 61)

Select mix for max R at RFI fundamental frequency NOT frequency of receiver.

Example:

for .1-10 MHz use mix 75/77

for 1-300 MHz use mix 31

for 20-250 MHz use mix 43

for 200-2000 MHz use mix 61

Most popular ham frequency mixes are 31, 43, 61, 75, 77.

Wrong or unknown mix will probably not work so.....

Know how to buy

How to buy Ferrites the **right** way!



RFI Solutions from KHz to GHz



Ferrite Split Beads
10 Pack -1/2" ID
RFI Range: 1-300 MHz
Mix 31
Single turn, each bead provides:
71Ω/5 MHz, 100Ω/10 MHz
156Ω/25 MHz, 260Ω/100 MHz,
260Ω/250 MHz

For: AC/DC Power, Coax, Ethernet, Audio/Video Cables

Multiple turns for best results

Part # FSB31-1/2-10

=

**BUY With
CONFIDENCE!!**

Product Labeling (Mix, Frequency, Impedance) + Known Vendor = Winner!

So let's recap RFI 101

Ferrite Use Recap

- Determine RFI interfering frequency & suspected Path
 - Choose proper mix (31, 43, 61, 75/77) to suppress RFI fundamental frequency
- Choose Topology (slip, snap, ring) to fit the Path “Antenna”
 - Install ferrites – retest for RFI suppression
 - Consider additional ferrites or Paths if RFI persists

Most popular Mix for HF is MIX 31 (1-300 MHz)
(Mix 75/77 for .1-10 MHz, Mix 61 for 200-2000 MHz)

How and where do you put the ferrite band aid for transmitter RFI?

Tip #1 - Install Transceiver, Linear Amp RFI Filters


Goal: Minimize SOURCE RFI from radio and amplifier “antennas”



Transceiver/Amp RFI Kits


Palomar RFI kits for all brands of transceivers and amplifiers

Transceiver RFI Kit

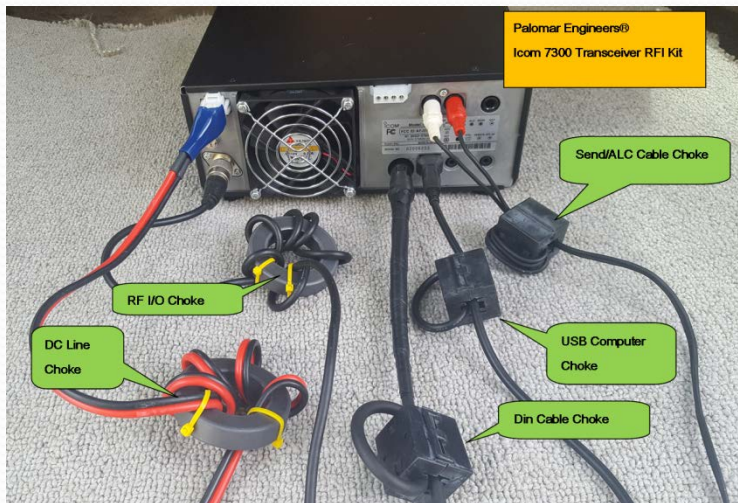

ICOM 7300

Linear Amplifier RFI Kit

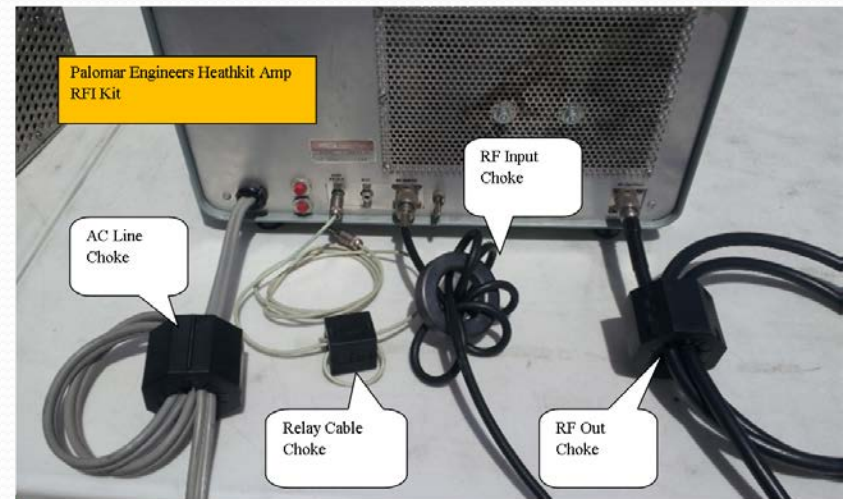

HEATHKIT SB220

Clean up the RFI **SOURCE** first – your radio and amp

Tip #2. Stop Transmit RFI current on coax braid


ALL coax fed antennas need a feed line
choke at the antenna feed point!!!!

OR

Your dipole will become a tripole
Your unipole (vertical) will become a dipole





Typical Coax Fed Antenna System

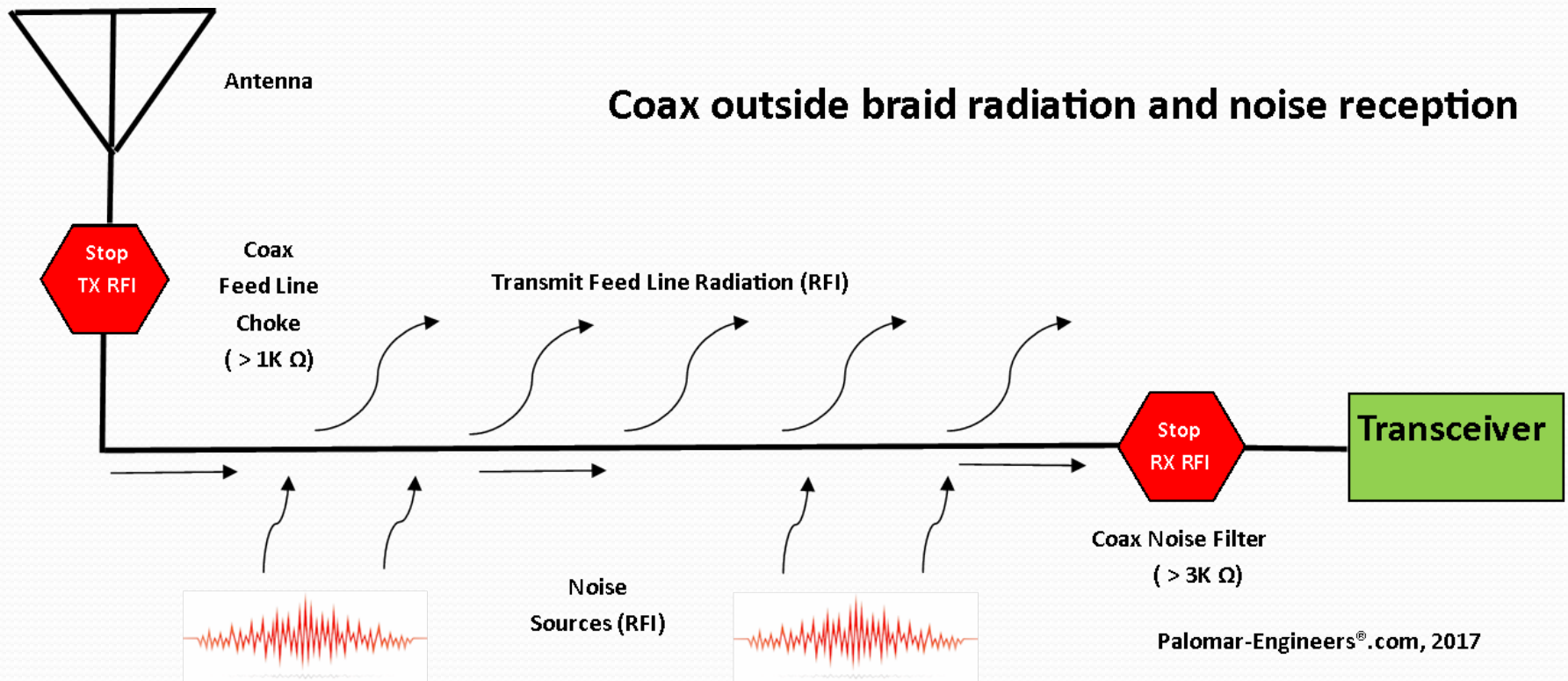


Technical requirements for feed line choke selection

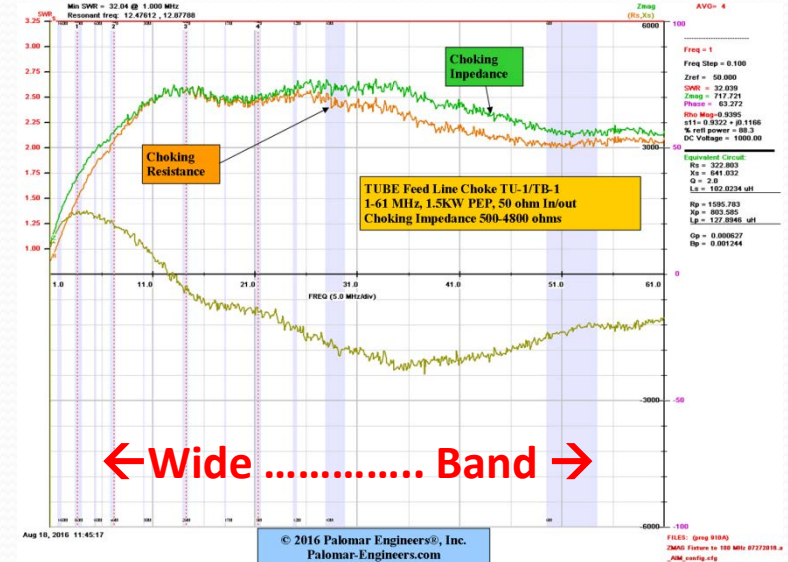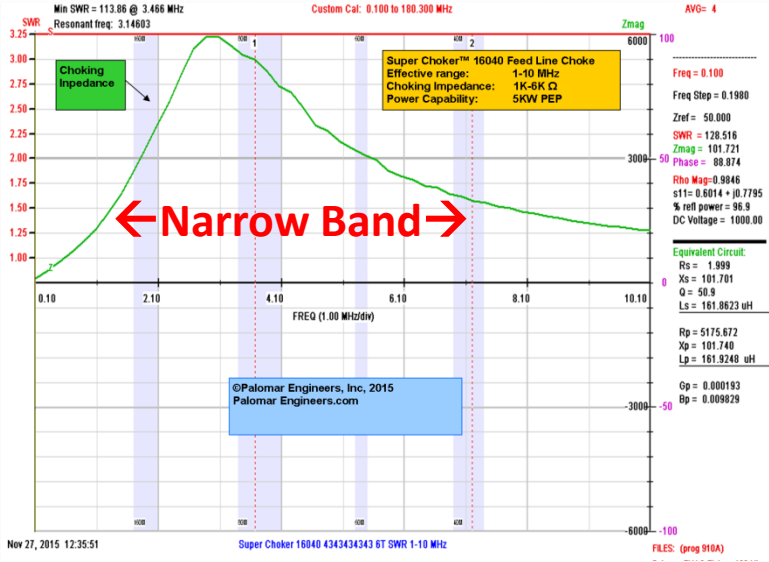Choose choking resistance > 500Ω over frequency range used



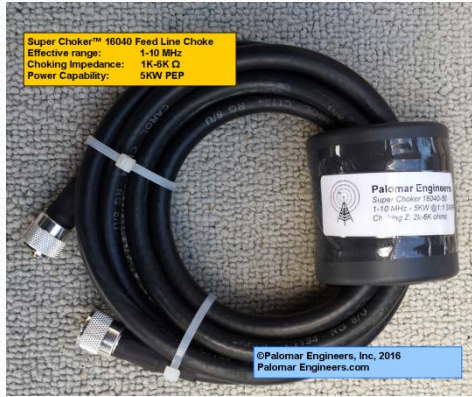Super Choker
 1-10 MHz >2K
 5KW PEP
 1K-6K Z
 3 pounds
 Verticals
 AM/RTTY
 Contesting



Line isolator
 1-160 MHz >2K, 1.5KW PEP, 1K-6K ZΩ, 1 pound. All coax lines, Optional ground, static bleeder

DO NOT BUY CHOKES with NO SPECS!

Tip #3. Install Coax Noise Filter to Suppress RX RFI


Less common mode noise current (RFI) = More DX!
How to select and install filters for maximum effect



Receive RFI Problem


- Symptoms: High noise levels, spurs, buzzes, periodic signals across bands

Typical Receive Chain Connections

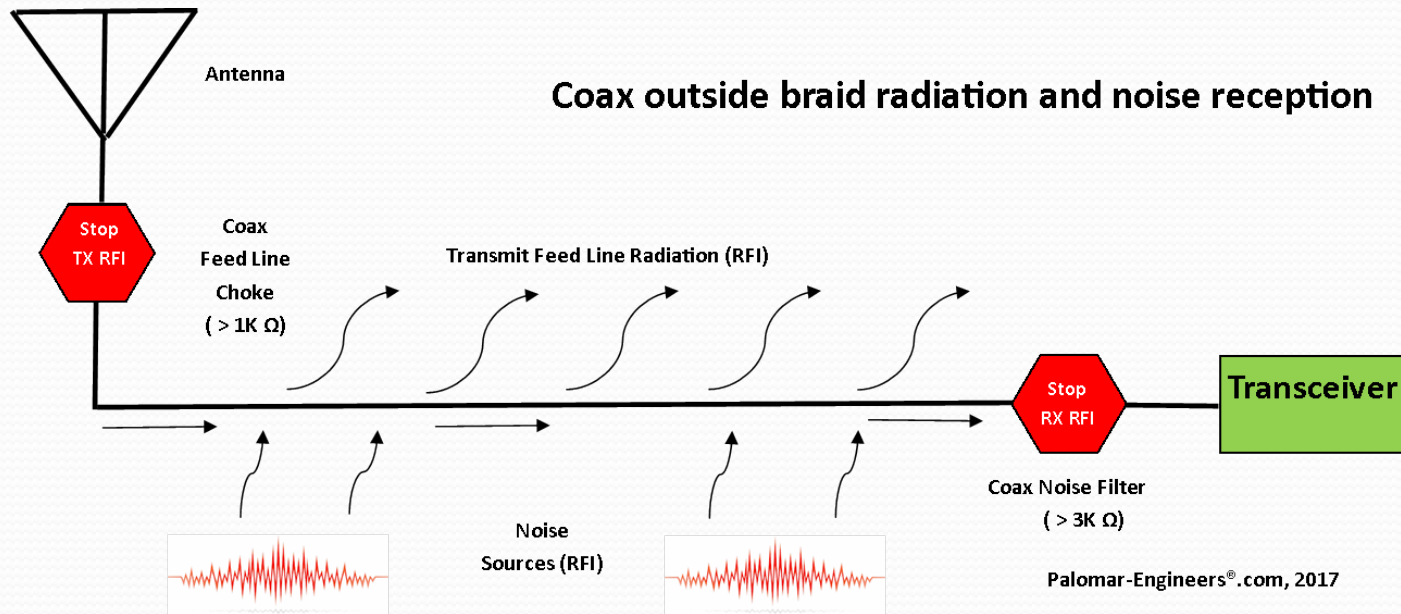

Coax Feed Line Noise Filters
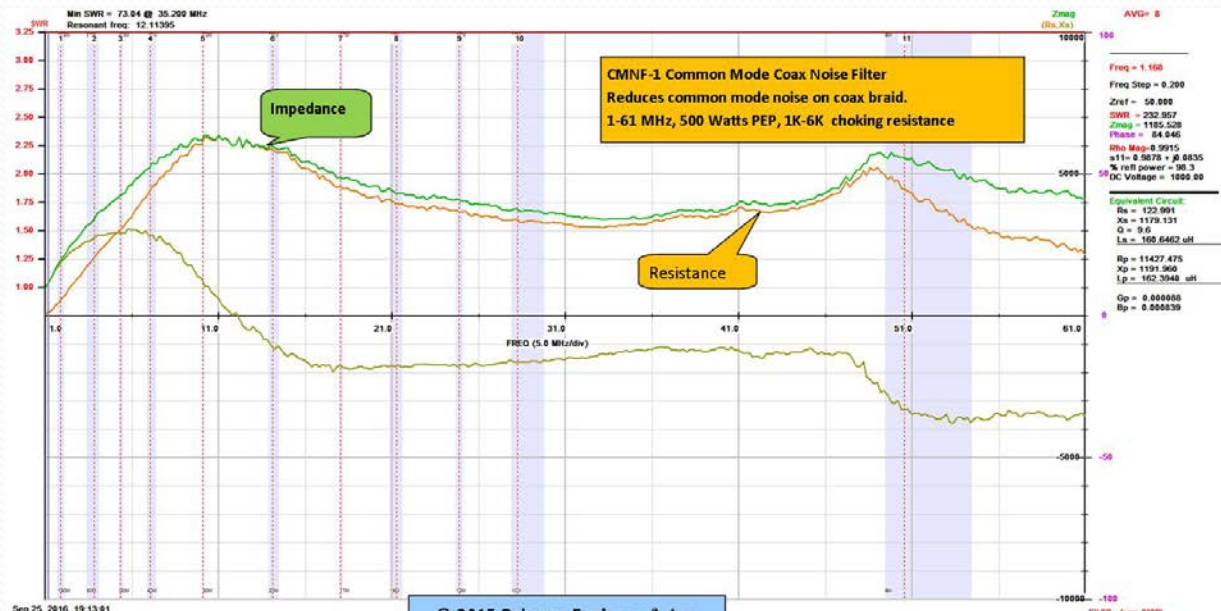
>>> One of the best kept secrets in ham radio!!! <<<



Placed at RADIO END of coax feed line to suppress common mode current on coax braid between antenna feed point choke and radio

Now AC/DC Filters


Tip #4. Install AC/DC Noise Filters

Lower Noise Floor = Higher SNR = More DX!
How to select and install filters for maximum effect

Goal is to reduce common mode RFI current superimposed on regular
signal INTO “receiver”



RFI – AC/DC Line Chokes

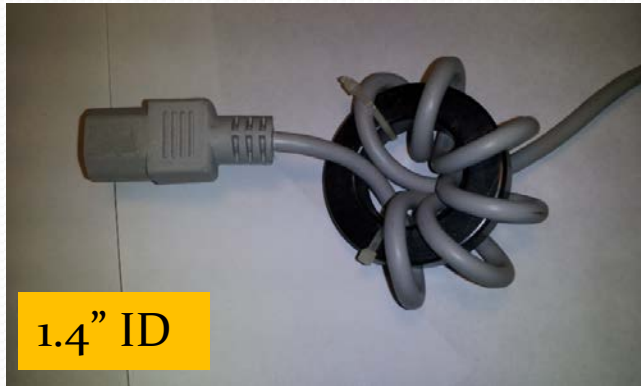

Choose mix frequency range and size to fit cable – use multiple turns

Wall Wart RFI Noise Reduction Kit

Wall Wart switching DC power supplies that plug into the AC power line plug and provide DC power to laptops, routers, battery chargers, cell phone chargers, etc are a known source of broadband RFI

A simple ferrite ring filter on the DC power line can help suppress the RFI noise affecting the device or keep the DC power cord from acting as an antenna and radiating RFI from the powered device.



RFI Filter on DC Cord



Economy 10 ring kit

Tip #5. Install Solution Specific RFI Kits

Our Goal: Minimize Transmit RFI to Home Electronics and Home
Electronics RFI to receiver

Garage Door Opener RFI Kit

Washer/Dryer/Refrigerator RFI Kits

Home Alarm RFI Kit

Computer Desktop, laptop, router RFI Kits

Home Theater A/V Systems



Neighborhood RFI Solutions

MY HOME or NEIGHBOR'S HOME



ALARM SYSTEM RFI



HOME THEATER RFI



COMPUTER RFI



MISCELLANEOUS RFI



GARAGE DOOR



TELEPHONE/DSL RFI

Recommendation: Use RFI kits for specific problems, have neighbor purchase and install – do not make mods to neighbors equipment! MOST problems are RFI picked up by AC power/phone lines so ferrite filters work well.

Prize Time

Prize Question #1

- What are 2 ways to increase the choking resistance of a ferrite filter choke?
 - A) Use high resistance wire and multiple turns on bead
 - B) Use multiple turns and double shield coax
 - C) Use multiple beads in series with multiple turns
 - D) Use mix 31 and mix 77 beads in series with a single turn

Prize Question #2

Mix 77 is used in which frequency range to suppress RFI common mode current?

- A) 1-300 MHz
- B) 200-2000 MHz
- C) .1-10 MHz
- D) 1-2000 MHz
- E) CB Band Only

Prize Question #3

TOP SECRET

- What is one of the best kept secrets in ham radio?
 - a) Ladder line has more loss than coax
 - b) A coax wound choke can cover all frequencies from 160-6 meters if the coax is long enough
 - c) All ferrites work on all frequencies, so buy the cheapest
 - d) Coax noise filters reduce common mode noise level in your receiver so you can hear more stations
 - e) All extra class hams go to heaven

Bonus Prize Question #4

- Which company is your best source for RFI solutions?



RFI Solutions from KHz to GHz

- Website: www.Palomar-Engineers.com
- Email: Sales@Palomar-Engineers.com
- Phone: 760-747-3343
- Bob Brehm, AK6R – Chief Engineer
- This presentation available on the website.