

ABC's of RFI for Hams



Bob Brehm, AK6R Chief Engineer Palomar-Engineers.com


SCDXC – 9/12/2024 This presentation available on website Copyright 2013-2024 Palomar Engineers, Inc.

Palomar Engineers Short History

- Founded in 1965 by Jack Althouse, K6NY (aka Kurt Sterba)
- Reorganized in 2013 as RFI Solutions/Antenna company
- **Objective:** Provide products that make radio communication more effective & enjoyable
- Product Line
 - Ferrite Core Products
 - Baluns, Ununs, Feedline Chokes & Coax Noise Filters
 - Antenna Systems (OCF, End Fed, Loop, Terminated)
 - RFI Solution Kits for Ham, Commercial, Household
 - Kurt Sterba Books/Downloads
- **Distribution:** Ham Radio Outlet, Direct, eBay
- Markets: Consumer, Commercial, and Military

Are you the **SOURCE** of RFI?




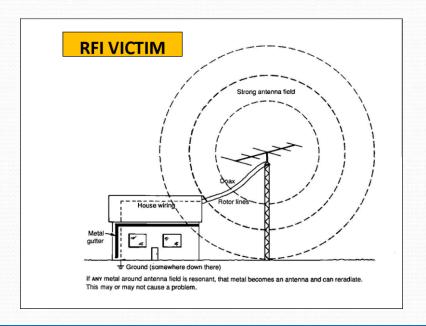


IT'S ALL YOUR FAULT WITH THAT BIG ANTENNA!

Maybe you got an award!



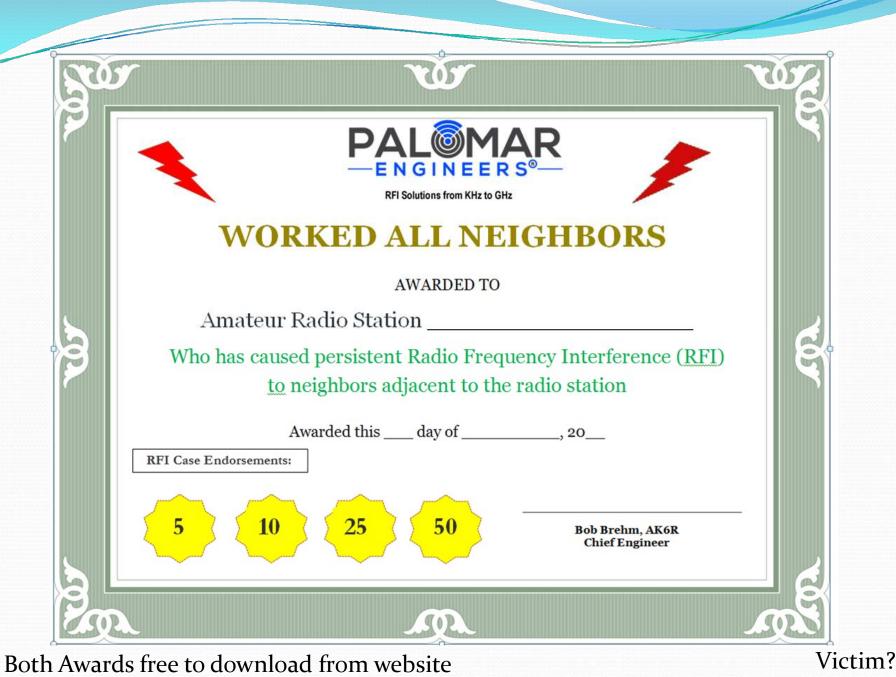

Are you a VICTIM of local RFI?

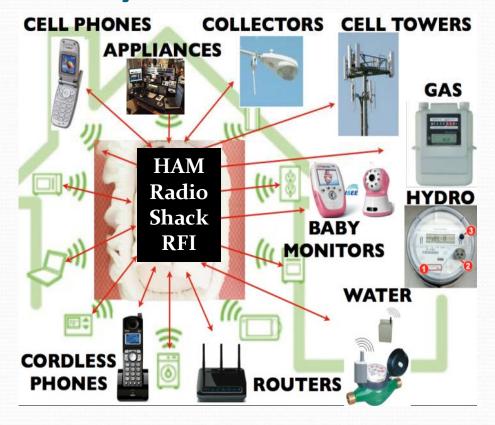

RFI Sources

- Ham Antenna
- Radiating Coax
- Electronic Devices
- Solar Systems
- Grow Lights
- HVAC motor
- Plasma TV
- DSL/Routers
- Switching power Supplies
- Washer/Dryer or other appliances

QRN - High Noise Floor - Weak Signals - NO DX - No fun!

Source or Victim – we can help!

Workshop Objectives





- Learn fundamentals of RFI <u>- identify symptoms</u>, <u>pinpoint</u> <u>causes</u> & <u>apply simple cures</u>
- What's a ferrite filter and how to choose & buy the right ferrite for your RFI issue
- How to use ferrites to solve the #1 RFI problem shared by all hams using coax-fed HF antennas
- How to use ferrites to <u>solve transmitter RFI problems</u>, <u>reduce your receiver noise</u> floor, and <u>keep your neighbor's</u> <u>and spouse happy!</u>
- Understand CONCEPTS with little or NO MATH required


Thinking cap time.....


What is RFI?



- A radio frequency (>100 KHz) disturbance that causes an electrical circuit to function improperly Common Sources
 - Sunspots, Cosmic noise, Lightning, atmospheric static, AC power lines (**no ferrite fix**)
 - "Transmitters" Ham, CB, AM/FM, electronic devices, speed controllers, inverters, switching power supplies, computer electronics, Cable/DSL/Ethernet (can use filters to fix)
- Common <u>Victims</u>
 - Any electronic device that malfunctions by acting as an unintended "receiver" of RFI

How RFI is Transferred

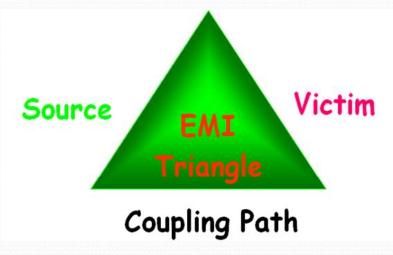


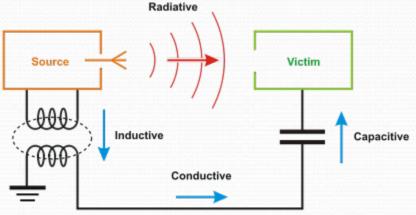

Source (antenna) and Victim (antenna) coupled via Path (all must be present to have RFI)

Multiple paths are very common:

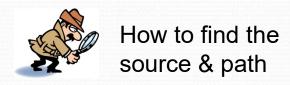- 1. Radiative air
- 2. Conductive wire(s)
- 3. Inductive wire
- 4. Capacitive wire



Typical RFI in your shack/home

- TX Symptoms caused by your transmitter or antenna
 - Hot microphone RF lip burns, distorted audio
 - Antennas don't tune correctly, high SWR, radiating coax
 - Your voice/transmission causes interference with consumer electronic devices acting as ham radio frequency "receivers" (e.g. computers, TV/audio system, security system, garage door opener, telephone, sprinkler systems, lights, etc.)
 - Spouse Alarm goes off!
- RX Symptoms caused by sources outside your radio
 - High receive noise level <u>not due</u> to atmospheric conditions
 - Birdies, chirps, buzzes, clicks, broadband noise on receiver
 - Distorted receiver audio

Typical RFI receiving "antennas"

- AM broadcast, 160-80-60-40-30 meter RFI look for long "antennas" AC power lines, telephone/DSL lines, satellite/cable coax, long Ethernet cables, antenna feed line coax shield, antenna control/rotor cables, 2nd story ground wires (avoid ¼ wavelength ground wires, e.g. 16 Feet)
- FM broadcast, 20 meter to 450 MHz RFI,— look for short "antennas" speaker wires, device interconnect cables, mic cables, short Ethernet cables
- "Antennas" pick up radiated or conducted RFI which induces a <u>common mode current on the SHIELD and ALL</u> unshielded "antenna" conductors from an RFI SOURCE

So how do we reduce this current?

Stop RFI = Minimize Current

I (RFI Current) = E (RFI induced voltage)/R (Choking resistance)

Shut down the SOURCE (Set E to zero)



- Choke the PATH (minimize I, increase R > 1000 Ω)
- Protect the VICTIM(Set R very high, >5000 Ω)

Objective: Minimize RFI current, I

Trivia Q: Why is current abbreviated with I and not C?

Ferrites are your friends to cure RFI



Ferrite Fundamentals

How to:

Select - Buy - Configure and Apply





Ferrite Topologies (Shapes)









Slip On Bead

Snap On Bead

Toroid or Ring

Fuzzy Ferret – not!

FERRITE CHARACTERISTICS

- •Cheap, easy to install, suppress RFI from 100 KHz 2 GHz
- •Work on all <u>conductive</u> paths (antenna & feed lines, AC/DC, I/O cables)
- •Lots of options in size, shape, frequency range to suppress RFI currents
- •Are effective if you understand <u>how ferrites work</u>, <u>how to choose the correct ferrite</u> and <u>where to install the ferrite</u> for a particular RFI problem


Ferrite characteristics can be used to reduce RFI common mode current


How do Ferrites Work?

(a)

Ferrites are frequency dependent "resistors"

Simple Equivalent Circuit

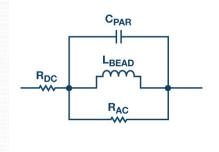


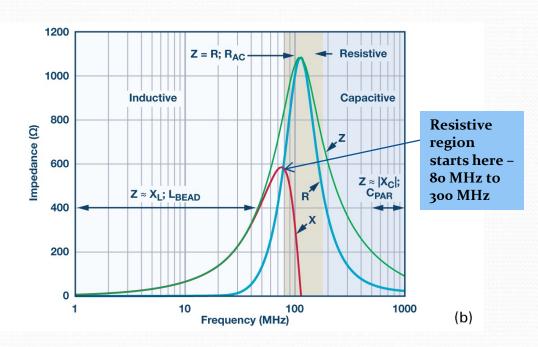

Ferrites are categorized by three response regions: inductive, resistive, and capacitive. To reduce high frequency interference (noise), the ferrite must be used in the resistive region where it acts like a resistor (R = F(MHz), which impedes the RF frequency noise (current) and dissipates it as heat.

How can resistance be increased?

Ferrites act like resistors-F(MHz)

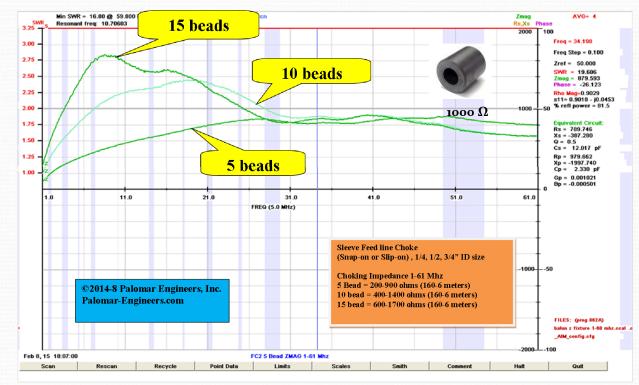

beads add resistance in series, but frequency dependent

higher choking R (up to 30 MHz in this example)

At 7 MHz:

 $5 \text{ beads} = 400\Omega$

 $10 \text{ bead} = 1000\Omega$

15 beads = 1600Ω

Feedline Chokes




Frequency (1-60 MHz) →

Impedance

Impedance (Z) = Resistance +/- Reactance

Ferrites have one more additional very useful property...

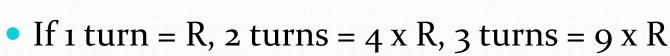Ferrite resistance increases as (turns thru center hole)²



- More R = less RFI wire current, I = less RFI radiated from wire or induced into wire. (I=E/R)
- General rule: choking R > 10X line impedance
- (e.g. > 500 Ω for 50 Ω cable but 5000 Ω is 10x better)








7 MHz: 100Ω (1 turn)

 900Ω (3 turn)

 4900Ω (7 turn)

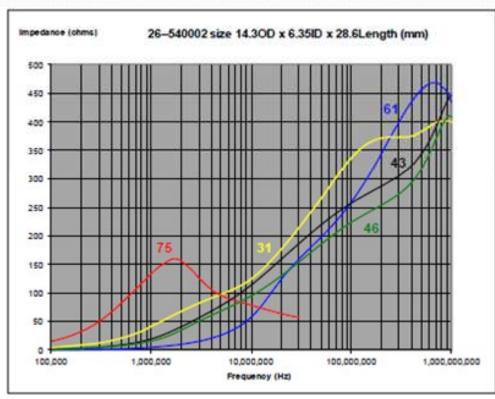Question: How do we choose the correct ferrite for the RFI frequency?

Ferrite composition (Mix) determines frequency range



Mix = chemical formula of the iron oxide with manganese-zinc (31, 75) or nickel-zinc (43, 61)

RULE:

Select mix for max R at RFI FUNDAMENTAL frequency NOT frequency of receiver.

Example:


for .1-5 MHz use mix 75 for 1-300 MHz use mix 31 for 20-250 MHz use mix 43 for 200-2000 MHz use mix 61

Most popular ham frequency mixes are 31, 43, 61, 75.

Select mix based on RFI Frequency example – multi-bead sleeve choke

Match RFI Frequency to Mix

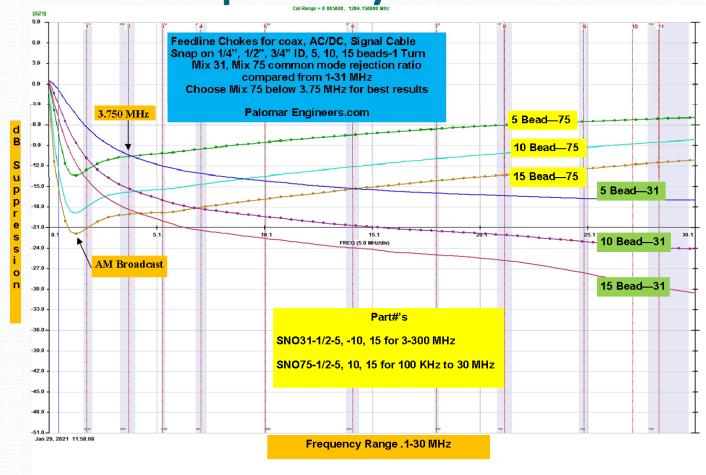Mix 75 up to 10 dB better under 3.75 MHz!




Selecting wrong or unknown mix will probably not work so..

How NOT to buy

How NOT to buy ferrites!



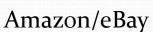



Swap meet

DON'T

BUY!!!

- NO Mix Designation
- NO Resistance/Impedance Range
- NO Frequency Range = No No No!
- <u>Like Buying a resistor with no color bands (unknown resistance)!</u>

Buying unknown ferrites is like buying a box of rocks - a waste of time and money!

Another Alternative?

How to buy Ferrites the right way!





Ferrite Split Bead 10 Pack -1/2" ID – Mix 31

RFI Range: 1-300 MHz Part#: FSB31-1/2-10

Single turn, each bead provides:

MHz	5	10	25	100	250
Ω	71	100	156	260	260

(2 turns=4XΩ, 3 turns =9XΩ, 4 turns = 16XΩ)
AC/DC/Coax/Audio-Video/Data Cables
Use multiple turns for best results

BUY With CONFIDENCE!!

Product Labeling (Mix, Frequency, Impedance) + Known Vendor = Winner!

So let's recap RFI 101

Ferrite Use Recap

- Determine RFI interfering frequency & suspected Path
- Choose proper mix (31, 43, 61, 75) to suppress RFI <u>fundamental</u> frequency
 - Choose Topology(slip-on, snap-on, ring) to fit the Path
 - Install ferrites on path retest for RFI suppression
 - Consider additional ferrites or paths if RFI persists

Most popular Mix for HF is MIX 31 (1-300 MHz) (Mix 75 for .1-5 MHz, Mix 61 for 200-2000 MHz)

Subtle Note: Mix frequency ranges shown are for <u>RFI suppression only. Mix</u> frequency ranges for use as impedance transformers (2:1, 4:1, 9;1, 49:1, etc) are different. NEVER use mix 31 for an impedance transformer as it has too much resistance and will heat up & easily saturate at low power.

How and where do you put the ferrite filter for transmitter RFI?

GOAL: STOP TRANSMIT RFI

Tip # 1: RFI Kits for HF Transceivers and Linear Amps

Tip # 2: Minimize coax cable radiation (HF or VHF)

Tip # 3: Install Solution Specific RFI Kits for VICTIMS

Transmit RFI Solution

Tip #1 - Install Transceiver, Linear Amp RFI Filters


Goal: Minimize SOURCE RFI <u>from</u> radio and amplifier cables acting as radiating "antennas"



RFI Filters for Transmitters/Amps

- Transmitter Amplifier Antenna RFI suppression
 - Choke <u>ALL</u> cables into/out of radios, amplifier, antenna tuners
 - Includes
 - Coax RF feed lines at antenna feed point to suppress TRANSMIT RFI
 - Rotor/Antenna Control lines
 - AC/DC power Lines including wall warts!
 - Computer all radio interconnects, AC power
 - Examples on next slides
 - Recommendation: Filter ALL cables to equipment using Palomar transceiver, amplifier and computer RFI kits with mix, sizes, instructions already pre-determined by brand.

Switch Mode Power Supply Filters

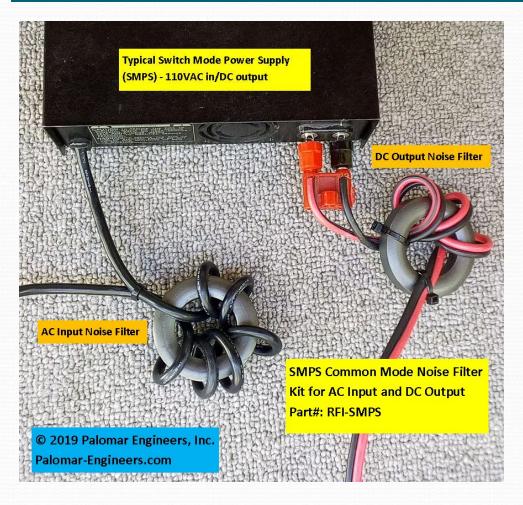

SMPS may act as an RFI transmitter and uses DC cable and AC power line as its "antennas" – so filter both lines using Mix 75 to suppress switching frequency fundamental (< 2MHz) and all harmonics in ham bands.


Part# RFI-SMPS

Transceiver Kits

Transceiver RFI Kits

Palomar has RFI kits for all brands of transceivers

Transceiver Standard RFI Kit

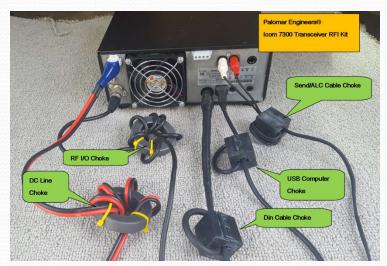

ICOM 7300

Transceiver Deluxe RFI Kit with NF



RULE: Clean up the RFI **SOURCE** first - your radio


Linear Amps too!

Linear Amplifier RFI Kits


Palomar has RFI kits for all brands of linear amps

Transceiver RFI Kit

Linear Amplifier RFI Kit

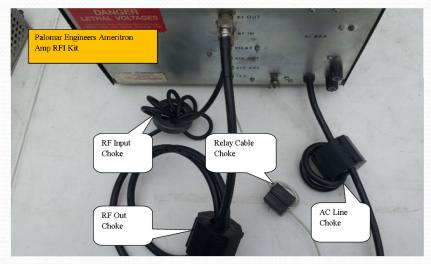

Ameritron 811

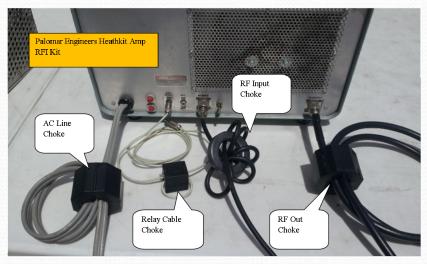

HEATHKIT SB220

Clean up the RFI **SOURCE** first – your radio and amp

Solution Kits for Tube and Solid State Amps

Now coax feed lines

Transmit RFI Solutions

Tip #2. Stop <u>Transmit</u> RFI current on coax braid




ALL coax fed antennas need a feed line choke at the antenna feed point!!!!!

OR

Your dipole will become a tripole or Your unipole (vertical) will become a dipole and your coax may radiate causing local RFI!

Is your Dipole a Tripole?

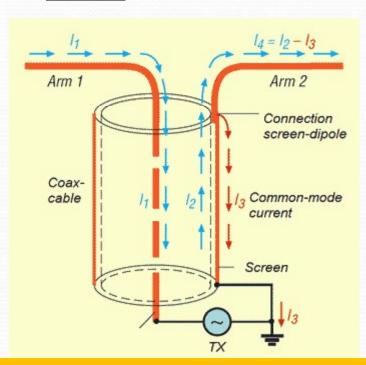 Coax <u>outside</u> of braid acts as extension of <u>transmitting</u> antenna and extra <u>receive</u> antenna




Coax cable has 3 conductors!

Coax <u>braid</u> is actually 2 conductors: 1 on the inside (normal RF signal), and 1 on the outside (common mode current) that turns a dipole into tripole on transmit or a second antenna on receive!

Goal is to reduce common mode current with a feed line choke to keep all transmit RF on antenna and use a coax noise filter to minimize noise into receiver.


FYI: 5% common mode braid current = 13.75 watt radiation at 1500 watts output, or 8 watts at 500 watts output or 3.5 watts at 100 watts output

Typical Coax Fed Antenna System

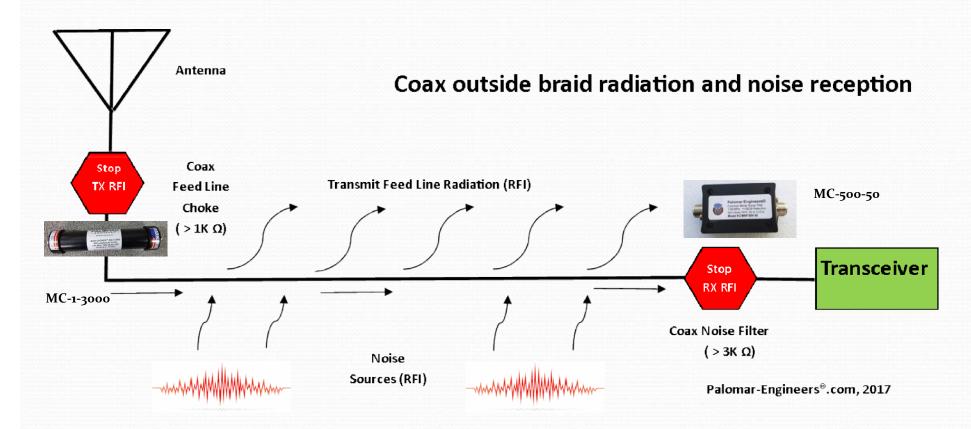

Technical requirements for feed line choke selection

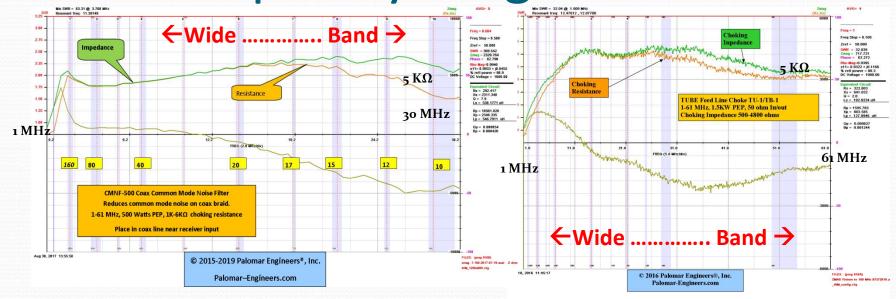Choose choking resistance > 1000Ω over frequency range used



Coax Noise Filter (CMNF-500-50)

1-65 MHz >2K 500 Watts PEP, Up to 38 dB reduction (6 "S" units of common mode noise gone!





Line isolator (part# MC-1-3000 – 3KW PEP)


1-61 MHz >2K, 3KW PEP, 1K-6K Z Ω , 1 pound. All coax lines, Optional ground, static bleeder, up to 38db suppression!

Same data measured on VNA as CMRR →

Choose choke with CMRR > 20 dB

over frequency range used

CMRR =
Common Mode
Rejection Ratio

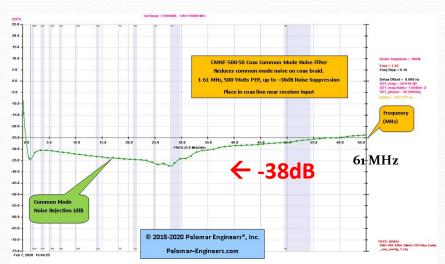



Coax Noise Filter (CMNF-500-50)

1-65 MHz >2K 500 Watts PEP, Up to 38 dB reduction (6 "S" units of common mode noise gone!



PALGOPTAR
ENGINEERS

PRACTICE TO SECURITY MC-1-3000
SOOL unbalanced In/Out
1-161 Minit 3000 Waits PER
Checking 2. Wedder.

Line isolator (part# MC-1-3000 – 3KW PEP)

1-61 MHz >2K, 3KW PEP, 1K-6K Z Ω , 1 pound. All coax lines, Optional ground, static bleeder, up to 49 dB suppression!

1 "S" unit = 6 dB, 36 dB = 6 "S" units

DO NOT BUY CHOKES with NO SPECS!

Chokes for Antenna Feed Point



3KW Maxi-Choker™ on beam



1:1 Balun = choke with balanced output – dipole antenna



Hybrid Baluns – 4:1 + 1:1 in same enclosure – OCF, Loop Antennas

Tip #3. Install Solution Specific RFI Victim Kits

Our Goal: Minimize Transmit RFI to Electronic Devices in your home or your neighbor's homes



OR



Neighbor RFI Strategy→

Neighbor's RFI Strategy

• Choke RFI SOURCE - YOU!



Ham's Strategy is different!

Ham's Solution to Neighbor's RFI

- Source (transmitter or antenna") Path Victim
 - Clean up your transmitter/shack first using techniques already discussed
- Assess Neighbor's Problem
 - Faulty device (device acting as receiver when not designed to be a radio receiver – e.g. Telephone, HDTV)
 - Determine frequency of "transmitter" that is causing the problem (may not be on all bands may not be you!)
 - Find the path (or paths) to the Victim (Receiver)
 - Choose the RFI choke kit for the frequency and path
 - Choke the path, protect the device (externally)!

SignalPen® – Simple RFI Detector



- SIGNALPEN™
- Self Powered Pencil Size RF Detector Light
 - 60 Hz to 1.2 GHz
- Milliwatts to Kilowatts Direct Contact or Inductive Detector, No Battery!
 - Proximity Range: .5-3Ft
 - Part# SIGNALPEN

Transmit RFI Solutions

MY HOME or NEIGHBOR'S HOME



ALARM SYSTEM RFI



MISCELLANEOUS RFI



HOME THEATER RFI



GARAGE DOOR



COMPUTER RFI



TELEPHONE/DSL RFI

Recommendation: Use RFI kits for specific problems, have neighbor purchase and install – <u>do not make mods to neighbors equipment!</u> MOST problems are RFI picked up by AC power/phone lines so ferrite filters work well.

TX RFI Recap

RFI proof your transmissions recap

- Determine frequency range of RFI and Path
- Install transceiver and amplifier RFI kits to suppress RFI
- Install a feed line choke in ALL antenna coax lines of your station at the antenna feed point with enough choking impedance at the frequency of use to minimize coax braid radiation
- Install AC/DC power filters on affected equipment and retest for RFI suppression
 - Consider additional filters and paths if RFI persists

If you need help

Call or email (sales@Palomar- Engineers.com) or view specific solutions at **Palomar-Engineers.com**

Transmit RFI Solution

GOAL: SUPPRESS RECEIVE RFI

Tip # 4: Install Coax Noise Filters if needed

Tip # 5: Identify & Suppress Local RFI/Noise Sources

Tip# 6: Isolate Antenna Switch coax braids



Receiver RFI Noise Strategy

- Assess S-P-V for the RFI You or someone else is source?
- PROTECT the VICTIM (Your receiver)
 - Ferrites on AC/DC cords, Wall Warts ring or snap on ferrites
 - Coax noise filters on antenna feed lines, ferrites on rotor lines
 - Ferrites on radio to computer interconnect cables
- ELIMINATE/ISOLATE the SOURCE
 - Choke AC/DC power to source, snap on ferrites for all I/O
- Call Palomar Engineers if you get stuck or need help

RFI – AC/DC Power Line Chokes










Choose mix frequency range and size to fit cable – <u>use max multiple turns</u>

Receive Coax RFI Problem

 Symptoms: High noise levels, spurs, buzzes, periodic signals across bands

Typical Receive Chain Connections

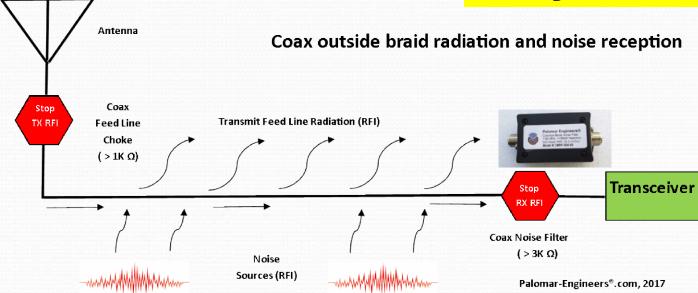Coax braid acts as 2nd receive antenna and combines with "real" signal at connector!



Simple common mode noise test $\rightarrow \rightarrow$

Receive RFI Solution

Tip #4. Install Coax Noise Filter to Suppress RX RFI

Less common mode noise current (RFI) = More DX! How to select and install filters for maximum effect

Quick Test for Common Mode RFI



Coax Center Conductor Only—measure noise level



Coax Center Conductor and outer shield — measure noise level. If higher, then you have common mode noise



Best kept secret!

Coax Noise Filter Specs




>>> One of the best kept secrets in ham radio!!! <<<

1.5KW or 5KW

500 Watts





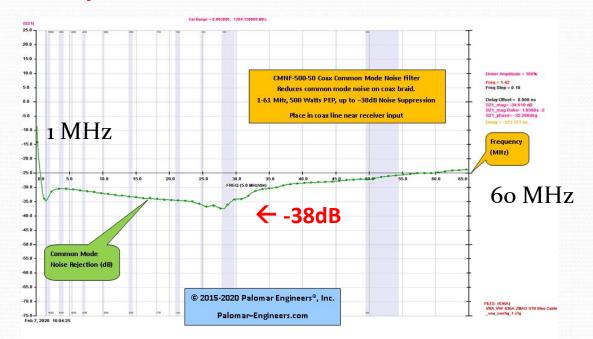


<u>Placed at RADIO END of coax feed line to suppress common mode</u> <u>current on coax braid between antenna feed point choke and radio</u>

1 "S" unit = 6 dB, -36dB = 6 "S" Units

Station Install Points

Coax Noise Filter Installation

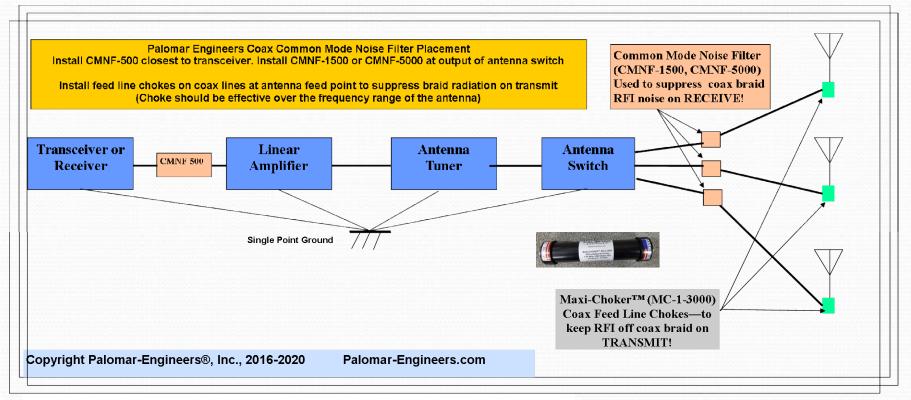


Where to Install

- Choke at antenna for <u>TRANSMIT</u> RFI
- Noise Filter at Antenna Switch for <u>RECEIVE</u> RFI
- Between Transceiver and Amplifier
- Single point ground system

Antenna Switch Solution

Antenna Switch Solution

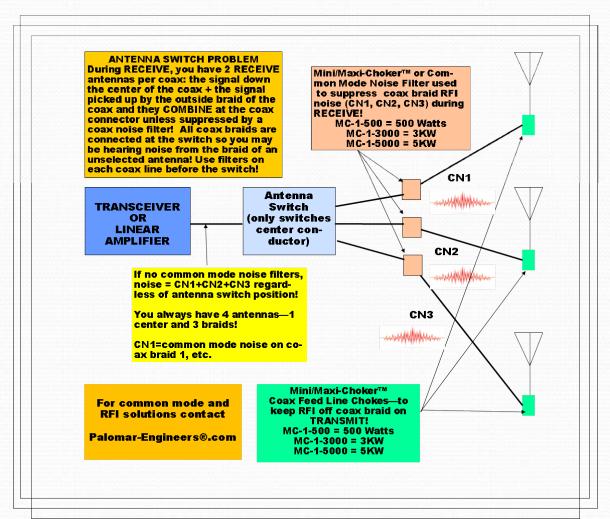



500 watt Coax Noise Filters 2 port switch = 3 RX antennas!




Coax Braid Isolators

RFI/Noise Fix for FLEX Station

Palomar Engineers®.com FLEX RADIO SYSTEM INSTALLATION DIAGRAM—SO2R OPTION RFI Kits Shown: RFI-FLEX-6400/6600, RFI-LA-FLEX, RFI-AT-FLEX-TG, RFI-AS-FLEX-AG Palomar Engineers Coax Common Mode Noise Filter Placement Install CMNF-500 closest to transceiver. Install CMNF-1500 or CMNF-5000 at output of antenna switch Use 3KW Maxi Chokers TM or CMNF-500 Coax Noise Filters to suppress coax braid noise Install feed line chokes on coax lines at antenna feed point to suppress braid radiation on transmit (Choke should be effective over the frequency range of the antenna) between antennas on receive! FLEX XCVR Power Genius Amp Tuner Genius-SO2R Antenna Genius **XCVR PGXL** FSB31-1/2 AC POWER **Coax Braid Isolators** Network LAN Hub DC Power LAN PTT used to key amp, otherwise use FSB31-1/2 on PTT lines

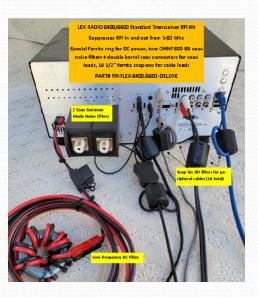Tuner Genius with 3 antenna outputs use another FSB31-1



Suppress RFI Receive Noise Recap

- Perform simple noise test on your radio
 - Unplug your antenna and see if all the noise goes away if not, noise is entering from another wire into radio – probably power supply – install transceiver RFI kit on all lines
 - Perform common mode test with antenna coax if noise increases when you screw in the outer coax connector you have common mode noise and need a coax noise filter. IF no change then ferrite filters won't help and you will have to kill the path or stop the SOURCE
 - If you have an antenna switch unplug all antennas and perform the above test on each antenna coax individually and install coax noise filters as needed
- Consider additional filters and paths if RFI persists

If you need help
Call or email (sales@Palomar- Engineers.com) or view specific solutions at
Palomar-Engineers.com

Receive RFI Solution

Transmit RFI Solution

Tip #7. Use Ferrite Combo RFI Kits for Newbies

Ferrite Combo Kits for Troubleshooting Multiple RFI Issues include <u>multiple ferrite shapes and sizes</u>

<u>or</u>

½" ID snap-ons and 1.4" ID rings are the most popular sizes and can be used to solve most ham radio HF RFI problems





Buy 9
Get 1
FREE!



Use Discount code "NEWBIE24" – get 10% off orders thru 12/31/2024

Test Time

Question #1

- What are the 2 best ways to increase the choking resistance of a ferrite filter?
- A) Use high resistance wire and multiple turns on bead
- B) Use multiple turns and double shield coax
- C) Use multiple beads in series with multiple turns
- D) Use mix 31 and mix 75 beads in series with a single turn

Question #2

Mix 61 is used in which frequency range to suppress RFI common mode current?

- A) 1-300 MHz
- B) 200-2000 MHz
- C) .15-5 MHz
- D) 1-2000 MHz
- E) CB Band Only

Question #3



- What is one of the best kept secrets in ham radio?
- a)Ladder line has more loss than coax
- b) A coax wound choke can cover all frequencies from 160-6 meters if the coax is long enough
- c) All ferrites work on all frequencies, so buy the cheapest
- d) Coax noise filters reduce common mode noise level in your receiver so you can hear more stations
- e) All extra class hams go to heaven

BONUS Question

Bonus Question #4

 Which company is your best source for RFI & HF Wire Antenna solutions?



RFI Solutions from KHz to GHz

- Website: Palomar-Engineers.com
- Email: Sales@Palomar-Engineers.com
- Phone: 760-747-3343
- Bob Brehm, AK6R Chief Engineer
- This presentation available on the website.