

Quick & Easy RFI Solutions




Bob Brehm, AK6R Chief Engineer Palomar-Engineers.com

YUMA Hamfest – February 2020 This presentation available on website Copyright 2013-2020 Palomar Engineers, Inc.

Are you the **SOURCE** of RFI?



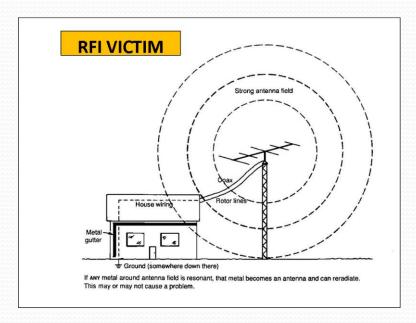


IT'S ALL YOUR FAULT WITH THAT BIG ANTENNA!

Maybe you got an award?



Are you a VICTIM of local RFI?

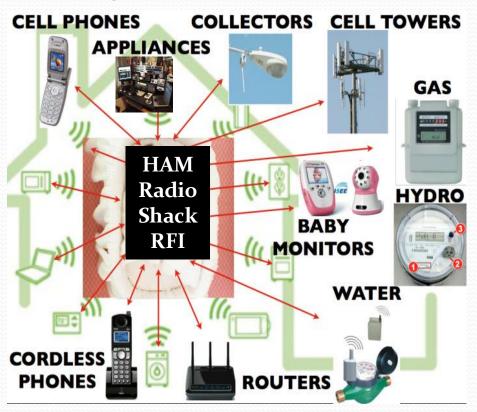

RFI Sources


- Ham Antenna
- Radiating Coax
- Electronic Devices
- Solar Systems
- Grow Lights
- HVAC motor
- Plasma TV
- DSL/Routers
- Switching power Supplies
- Washer/Dryer or other appliances

QRN - High Noise Floor - Weak Signals - NO DX - No fun!

What is RFI?

- A radio frequency (>100 KHz) disturbance that causes an electrical circuit to function improperly Common Sources
 - Sunspots, Cosmic noise, Lightning, atmospheric static, AC power lines (no fix)
 - "Transmitters" -Ham, CB, AM/FM, electronic devices, speed controllers, inverters, switching power supplies, computer electronics, Cable/DSL/Ethernet (can use filters to fix)
- Common Victims
 - Any electronic device that malfunctions by acting as an unintended "receiver" of RFI

How RFI is Transferred

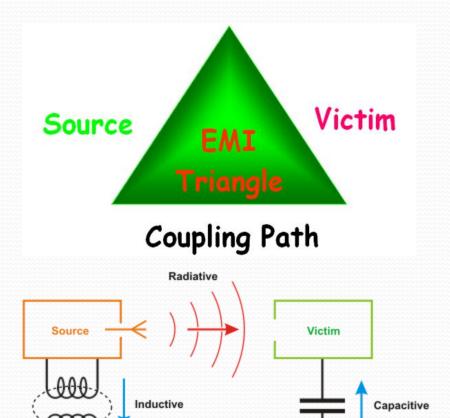

Conductive

Source (antenna) and Victim (antenna) coupled via Path (all must be present to have RFI)

Multiple paths are very common:

- 1. Radiative air
- 2. Conductive wire(s)
- 3. Inductive wire
- 4. Capacitive wire



Typical RFI in your shack/home

- TX Symptoms caused by your transmitter or antenna
 - Hot microphone RF lip burns, distorted audio
 - Antennas don't tune correctly, high SWR, radiating coax
 - Your voice/transmission causes interference with consumer electronic devices acting as ham radio frequency "receivers" (e.g. computers, TV/audio system, security system, garage door opener, telephone, sprinkler systems, lights, etc.)
 - Spouse Alarm goes off!



- **RX Symptoms** caused by <u>sources outside your radio</u>
 - High receive noise level <u>not due</u> to atmospheric conditions
 - Birdies, chirps, buzzes, clicks, broadband noise on receiver
 - Distorted receiver audio

Typical RFI receiving "antennas"

- AM broadcast, 160-80-60-40-30 meter RFI look for long "antennas" AC power lines, telephone/DSL lines, satellite/cable coax, long Ethernet cables, antenna feed line coax shield, antenna control/rotor cables, 2nd story ground wires (avoid ¼ wavelength ground wires)
- FM broadcast, 20 meter to 450 MHz RFI,— look for short "antennas" speaker wires, device interconnect cables, mic cables, short Ethernet cables
- "Antennas" pick up radiated or conducted RFI which induces a <u>common mode current on ALL unshielded</u> "antenna" conductors from an RFI SOURCE

Stop RFI = Minimize Current

I (RFI Current) = E (TX voltage)/R (Choking resistance)

Shut down the SOURCE (Set E to zero)



- Choke the PATH (minimize E, increase R)
- Protect the VICTIM(Set R very high)

Objective: Minimize RFI current, I

Trivia Q: Why is current abbreviated with I and not C?



Ferrite Fundamentals

How to:

Select - Buy - Configure and Apply



Ferrite Topologies (Shapes)









Slip On Bead

Snap On Bead

Toroid or Ring


Fuzzy Ferret – not!

CHARACTERISTICS

- •Cheap, easy to install, suppress RFI from 100 KHz 2 GHz
- •Work on all <u>conductive</u> paths (antenna feed line, AC/DC, I/O cables)
- •Lots of options in size, shape to suppress most RFI path currents
- •Are effective if you understand <u>how ferrites work</u>, <u>how to choose the correct ferrite</u> and <u>where to install the ferrite</u> for a particular RFI problem

Ferrite characteristics can be used to reduce RFI common mode current

Ferrites act like resistors (ΔF)

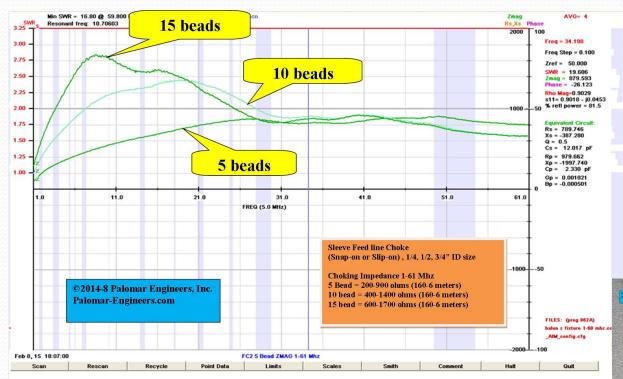

Frequency →

beads in series =

higher choking R (up to 30 MHz)

At 7 MHz:

 $5 \text{ beads} = 400\Omega$

 $10 \text{ bead} = 1000\Omega$

15 beads = 1600Ω



Ferrite resistors increase as (turns)²

- If 1 turn = R, 2 turns = 4 x R, 3 turns = 9 x R
- More R = less RFI wire current = less RFI radiated from wire or induced into wire. (I=E/R)
- General rule: choking R > 10X line impedance
- (e.g. > 500 Ω for 50 Ω cable but 5000 Ω is 10x better)








7 MHz: 100Ω 900Ω 2500 Ω

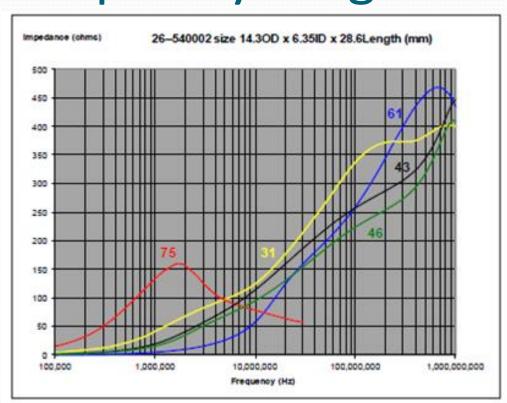Question: How do we choose the correct ferrite for the RFI frequency?

Ferrite "Mix" determines effective frequency range



Mix = chemical formula of the iron oxide with manganese-zinc (31, 75) or nickel-zinc (43, 61)

Select mix for max R at RFI fundamental frequency NOT frequency of receiver.

Example:

for .1-10 MHz use mix 75 for 1-300 MHz use mix 31 for 20-250 MHz use mix 43 for 200-2000 MHz use mix 61

Most popular ham frequency mixes are 31, 43, 61, 75.

Wrong or unknown mix will probably not work so......

Know how to buy

How NOT to buy ferrites!







BUY!!!

- NO Mix Designation
- NO Resistance/Impedance Range
- NO Frequency Range = No No No!

Buying unknown ferrites is like buying a box of rocks - a waste of time and money!

Another Alternative?

How to buy Ferrites the right way!





Ferrite Split Bead 10 Pack -1/2" ID – Mix 31 RFI Range: 1-300 MHz

Part#: FSB31-1/2-10

| Single | turn, | each | bead | provides: |
|--------|-------|------|------|-----------|
| | | | | |

| | | 10 | | | |
|---|----|-----|-----|-----|-----|
| Ω | 71 | 100 | 156 | 260 | 260 |

(2 turns=4XΩ, 3 turns =9XΩ, 4 turns = 16XΩ)
AC/DC/Coax/Audio-Video/Data Cables
Use multiple turns for best results



Product Labeling (Mix, Frequency, Impedance) + Known Vendor = Winner!

Ferrite Use Recap

- Determine RFI interfering frequency & suspected Path
- Choose proper mix (31, 43, 61, 75) to suppress RFI <u>fundamental</u> frequency
 - Choose Topology(slip, snap, ring) to fit the Path "Antenna"
 - Install ferrites retest for RFI suppression
 - Consider additional ferrites or Paths if RFI persists

Most popular Mix for HF is MIX 31 (1-300 MHz) (Mix 75 for .1-10 MHz, Mix 61 for 200-2000 MHz)

How and where do you put the ferrite band aid for transmitter RFI?

GOAL: STOP TRANSMIT RFI

Tip # 1: RFI Kits for HF Transceivers and Linear Amps

Tip # 2: Minimize coax cable radiation (HF or VHF)

Tip # 3: Install Solution Specific RFI Kits for VICTIMS

Transmit RFI Solution

Tip #1 - Install Transceiver, Linear Amp RFI Filters

Goal: Minimize SOURCE RFI from radio and amplifier "antennas"



RFI Filters for Transmitters/Amps


- Transmitter Amplifier Antenna RFI suppression
 - Choke <u>all</u> cables into/out of radios, amplifier, antenna tuners
 - Includes
 - ALL Coax RF feed lines or common line of coax switch
 - Rotor/Antenna Control lines
 - AC/DC power Lines including wall warts!
 - Computer all radio interconnects, AC power
 - Examples on next slides
 - Recommendation: Filter ALL power cables to equipment and buy Palomar transceiver, amplifier and computer RFI kits with mix, sizes, instructions already pre-determined.

Transceiver/Amp RFI Kits


Palomar has RFI kits for all brands of transceivers and amplifiers

Transceiver RFI Kit

Linear Amplifier RFI Kit

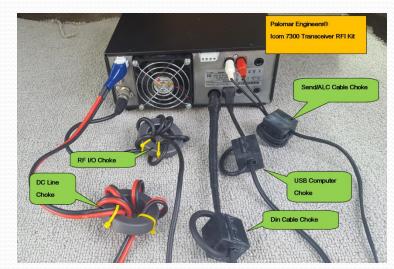

ICOM 7300

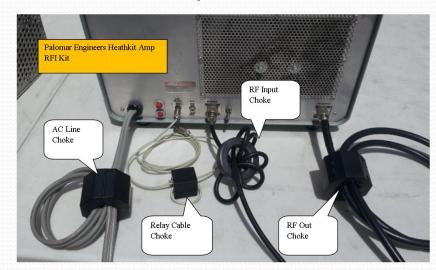

HEATHKIT SB220

Clean up the RFI **SOURCE** first – your radio and amp

Tip #2. Stop <u>Transmit</u> RFI current on coax braid




ALL coax fed antennas need a feed line choke at the antenna feed point!!!!!

OR

Your dipole will become a tripole or Your unipole (vertical) will become a dipole and your coax will radiate causing local RFI!

Is your Dipole a Tripole?

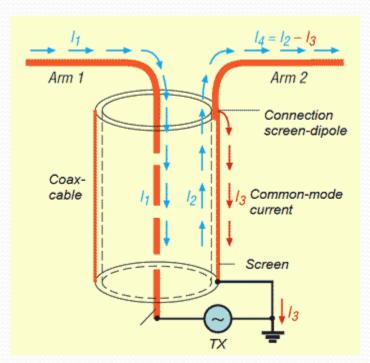 Coax <u>outside</u> of braid acts as extension of <u>transmitting</u> antenna and extra <u>receive</u> antenna




<u>Coax cable has 3 conductors!</u>

Coax <u>braid</u> is actually 2 conductors: 1 on the inside (normal RF signal), and 1 on the outside (common mode current) that turns a dipole into tripole on transmit or a second antenna on receive!

Goal is to reduce common mode current with a feed line choke to keep all transmit RF on antenna and use a coax noise filter to minimize noise into receiver.

FYI: 1% common mode braid current = 2.75 watt radiation at 1500 watts input, or 1.6 watts at 500 watts input or .7 watts at 100 watts input


Typical Coax Fed Antenna System

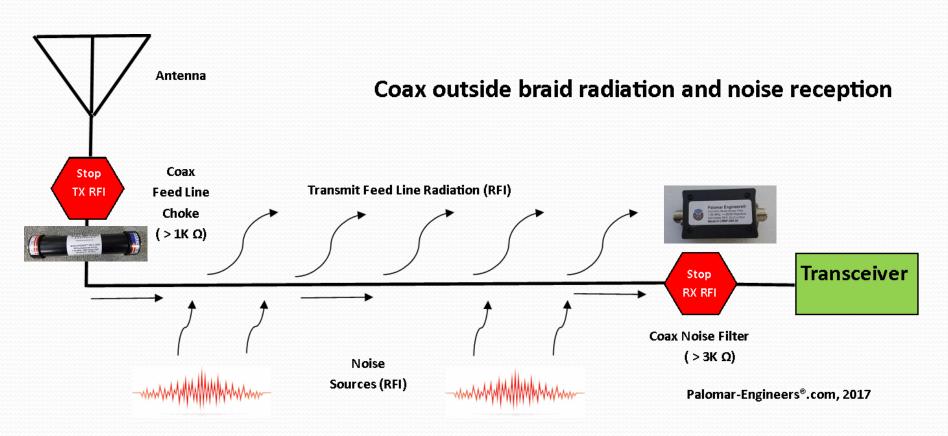

Technical requirements for feed line choke selection

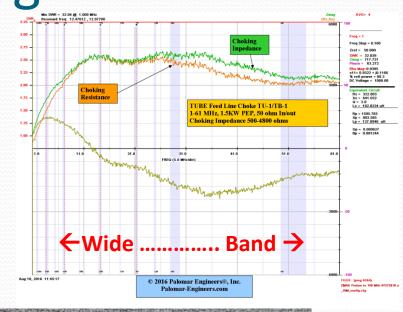Choose choking resistance $> 500\Omega$ over frequency range used





Super Choker 1-10 MHz >2K 5KW PEP 1K-6K Z 3 pounds Verticals AM/RTTY

Contesting







Line isolator

1-61 MHz >2K, 3KW PEP, 1K-6K Z Ω , 1 pound. All coax lines, Optional ground, static bleeder, up to 38db suppression!

DO NOT BUY CHOKES with NO SPECS!

Simple DIY Feed Line Chokes

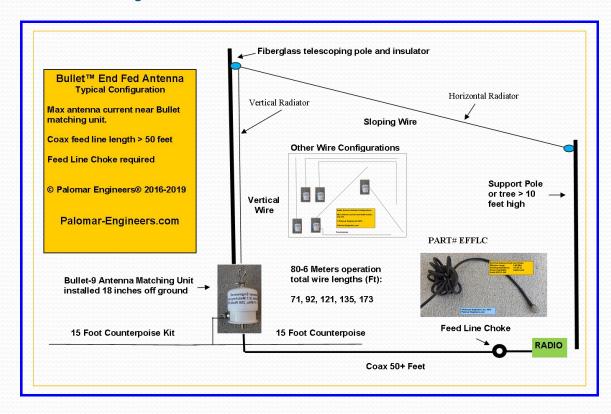

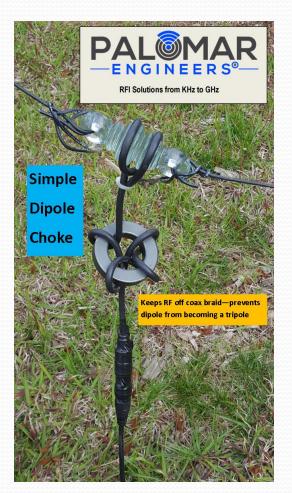

Use 1.4" ID Ring with multiple turns

Tip #3. Install Solution Specific Victim RFI Kits

Our Goal: Minimize Transmit RFI to Home Electronics and Home Electronics RFI to receiver

Garage Door Opener RFI Kit Washer/Dryer/Refrigerator RFI Kits Home Alarm RFI Kit Computer Desktop, laptop, DSL/Router RFI Kits Home Theater A/V Systems, Satellite Boxes Sprinkler Systems



Transmit RFI Solutions

MY HOME or NEIGHBOR'S HOME



ALARM SYSTEM RFI



MISCELLANEOUS RFI



HOME THEATER RFI



GARAGE DOOR



COMPUTER RFI



TELEPHONE/DSL RFI

Recommendation: Use RFI kits for specific problems, have neighbor purchase and install – do not make mods to neighbors equipment! MOST problems are RFI picked up by AC power/phone lines so ferrite filters work well.

RX Solutions

GOAL: SUPPRESS RECEIVE RFI

Tip # 4: Install Coax Noise Filters

Tip # 5: Identify & Suppress Local RFI/Noise Sources




Receive RFI Problem

Symptoms: High noise levels, spurs, buzzes, periodic signals across bands

2nd receive antenna!

Typical Receive Chain Connections

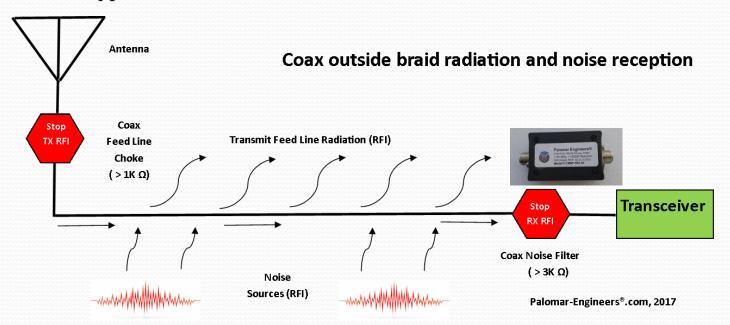

Receive RFI Solution

Tip #4. Install Coax Noise Filter to Suppress RX RFI

Less common mode noise current (RFI) = More DX! How to select and install filters for maximum effect

Quick Test for Common Mode RFI




Coax Center Conductor Only—measure noise level



Coax Center Conductor and outer shield — measure noise level. If higher, then you have common mode noise



Coax Noise Filter Installation

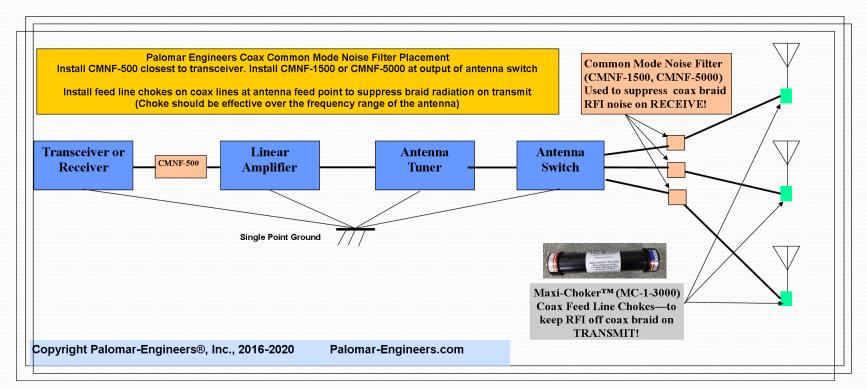

Where to Install

- Choke at antenna for <u>TRANSMIT</u> RFI
- Noise Filter at Antenna Switch RX RFI
- Between Transceiver and Amplifier
- Single point ground system

Antenna Switch Problem



Coax Noise Filter Comparisons→

Coax Noise Filter Comparison

OK



Better



Best



Snap On Choke 500-1000 Ω 1-2 "S" Units

Ring Choke ${}_{1}\text{K}-{}_{2}\text{K}\Omega$ 2-4 "S" Units

Noise Filter ${}_{2}$ K- ${}_{6}$ K Ω 3- ${}_{6}$ "S" Units

Criteria to Consider

- Adequate Choking Impedance (Z) > 500 Ω
- Effective Frequency Range where $Z>500 \Omega$
- Sufficient Power Rating (PEP, Digital)
- Physical Size/Weight/Coax Diameter


Coax Noise Filter Specs


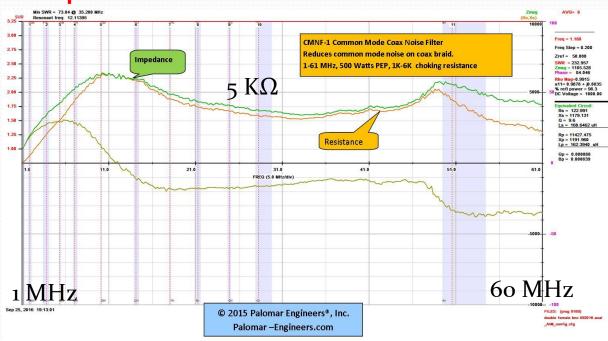
>>> One of the best kept secrets in ham radio!!! <<<







.5KW

Placed at RADIO END of coax feed line to suppress common mode current on coax braid between antenna feed point choke and radio

Tip #5. Install AC/DC Noise Filters


Lower Noise Floor = Higher SNR = More DX! How to select and install filters for maximum effect

Goal is to reduce common mode RFI current from power supply



RFI – AC/DC Line Chokes



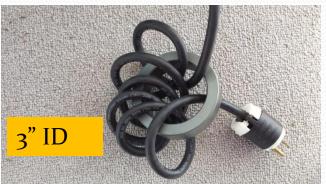






Choose mix frequency range and size to fit cable – use multiple turns

Switch Mode Power Supply Filters

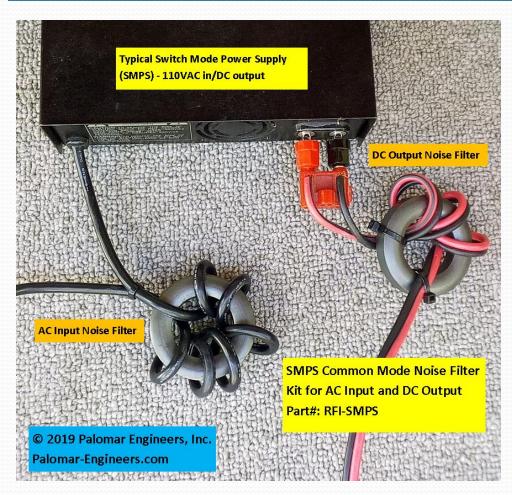

SMPS acts as RFI transmitter and uses DC cable and AC power line as its "antennas" – so filter both lines

Wall Wart RFI Noise Reduction Kit

Wall Wart switching DC power supplies that plug into the AC power line plug and provide DC power to laptops, routers, battery chargers, cell phone chargers, etc are a <u>known source of broadband RFI</u>

A <u>simple ferrite ring filter on the DC power line can help suppress the RFI noise</u> affecting the device or keep the DC power cord from acting as an antenna and radiating RFI from the powered device.



RFI Filter on DC Cord



Economy 5 or 10 ring kit

Transmit RFI Solution

Tip #6. Use Ferrite Combo RFI Kits for Newbies

Ferrite Combo Kits for Troubleshooting Multiple RFI Issues include <u>multiple ferrite shapes and sizes</u>

<u>or</u>

½" ID snap-ons and 1.4" ID rings are the most popular sizes and can be used to solve most ham radio HF RFI problems









Prize Question #1

 What are the 2 best ways to increase the choking resistance of a ferrite filter?

- A) Use high resistance wire and multiple turns on bead
- B) Use multiple turns and double shield coax
- C) Use multiple beads in series with multiple turns
- D) Use mix 31 and mix 75 beads in series with a single turn

Prize Question #2

Mix 75 is used in which frequency range to suppress RFI common mode current?

- A) 1-300 MHz
- B) 200-2000 MHz
- C) .15-10 MHz
- D) 1-2000 MHz
- E) CB Band Only

Prize Question #3



- What is one of the best kept secrets in ham radio?
- a)Ladder line has more loss than coax
- b) A coax wound choke can cover all frequencies from 160-6 meters if the coax is long enough
- c) All ferrites work on all frequencies, so buy the cheapest
- d) Coax noise filters reduce common mode noise level in your receiver so you can hear more stations
- e) All extra class hams go to heaven

BONUS Question

Bonus Prize Question #4

Which company is your best source for RFI solutions?



RFI Solutions from KHz to GHz

- Website: www.Palomar-Engineers.com
- Email: Sales@Palomar-Engineers.com
- Phone: 760-747-3343
- Bob Brehm, AK6R Chief Engineer
- This presentation available on the website.